 


Circuits avec interrupteurs commandés pour les $\neq$ portes logiques


chE3

a) une entrée E

si $E = 0$




si $E = 1$

 


CCL: porte NOT

b) deux entrées A et B


si $A = 0 = B$

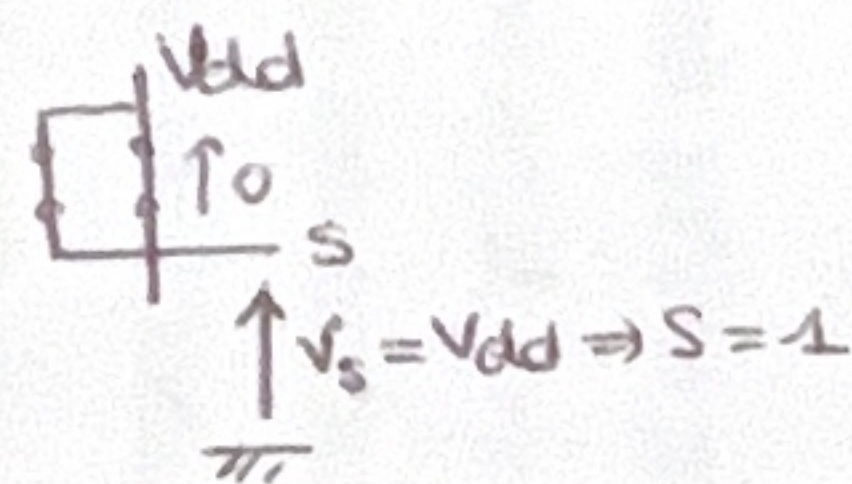


si $A = 0$
 $B = 1$

 

si $A = 1$
 $B = 0$

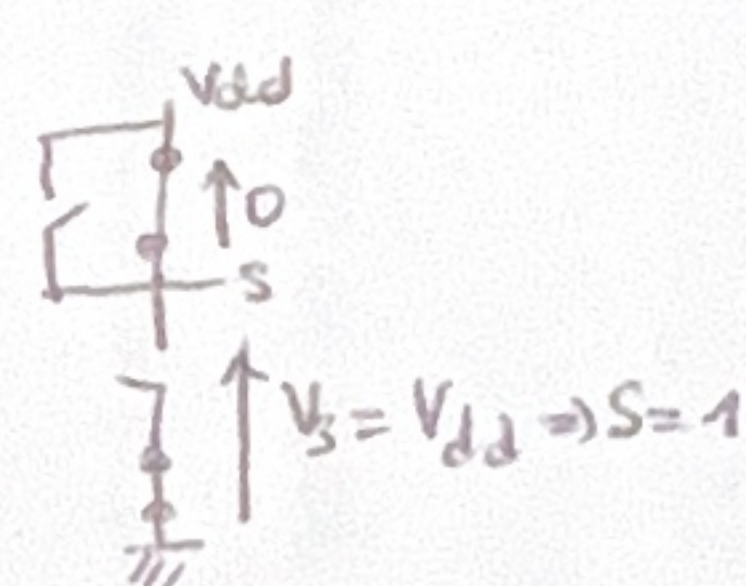

si $A = 1 = B$

 


A	B	S
0	0	1
0	1	1
1	0	1
1	1	0


CCL: porte NAND

c) deux entrées A et B


si $A = 0 = B$

 


si $A = 0$
 $B = 1$

 

si $A = 1$
 $B = 0$

 

si $A = 1 = B$

 


A	B	S
0	0	1
0	1	0
1	0	0
1	1	0


CCL: porte NOR

d) deux entrées A et B


si $A = 0 = B$

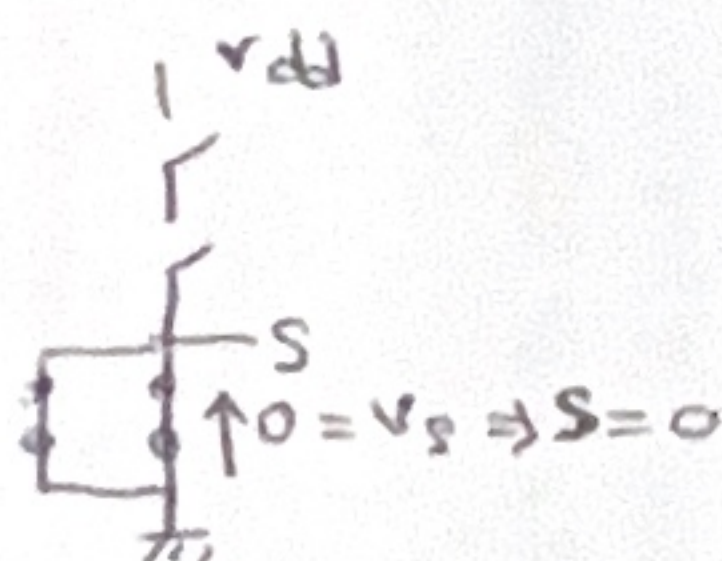


si $A = 0$
 $B = 1$

 

si $A = 1$
 $B = 0$

 

si $A = 1 = B$

 


A	B	S
0	0	0
0	1	0
1	0	0
1	1	1


CCL: porte AND

e) deux entrées A et B


si $A=0=B$

 


si $A=0$
 $B=1$

 

si $A=1$
 $B=0$

 

si $A=1=B$

 

A	B	S
0	0	0
0	1	1
1	0	1
1	1	1

CCL : porte OR