

RLC série

1 RLC série

$u_L + u_R + u_C = e$ soit $L \frac{di}{dt} + Ri + u_C = e$ soit

$$LC \frac{d^2 u_C}{dt^2} + RC \frac{du_C}{dt} + u_C = e$$

$\Delta = R^2 C^2 - 4LC$ et la résistance critique est celle pour laquelle $\Delta = 0$ soit $R_c = 2\sqrt{\frac{L}{C}}$

```
[6]: R,L,C,E=50,32e-3,100e-9,5
      Rc=2*(L/C)**0.5
      print(Rc)
```

1131.370849898476

$$\frac{d^2 u_C}{dt^2} = \frac{e - u_C - RC \frac{du_C}{dt}}{LC}$$

donc

$$\begin{cases} \frac{du_C}{dt} = v_C \\ \frac{dv_C}{dt} = \frac{e - u_C - RC v_C}{LC} \end{cases}$$

```
[7]: import numpy as np
      import matplotlib.pyplot as plt
      T0=2*np.pi*np.sqrt(L*C)
      tsim=10*T0
      pas=T0/1000
      N=int(tsim/pas)
      tab_t=np.zeros(N+1)
      tab_uc=np.zeros(N+1)
      tab_ducdt=np.zeros(N+1)
      tab_t[0],tab_uc[0],tab_ducdt[0]=0,E,0
      def derivee2(uc,ducdt,t):
          return (0-uc-R*C*ducdt)/(L*C)
      for i in range(N):
          tab_t[i+1]=tab_t[i]+pas
          tab_uc[i+1]=tab_uc[i]+pas*tab_ducdt[i]
          tab_ducdt[i+1]=tab_ducdt[i]+pas*derivee2(tab_uc[i],tab_ducdt[i],tab_t[i])
```

```


tab_i=C*tab_ducdt
tab_ur=R*tab_i
tab_ul=-tab_uc-tab_ur

```

```

[2]: plt.figure()
plt.plot(tab_t,tab_uc,label="uC")
plt.plot(tab_t,tab_ur,label="uR")
plt.plot(tab_t,tab_ul,label="uL")
plt.legend()
plt.ylabel("(V)")
plt.xlabel("t(s)")
plt.title("Tensions pour L=32mH, C=100nF, R=50Ω")
plt.show()

```

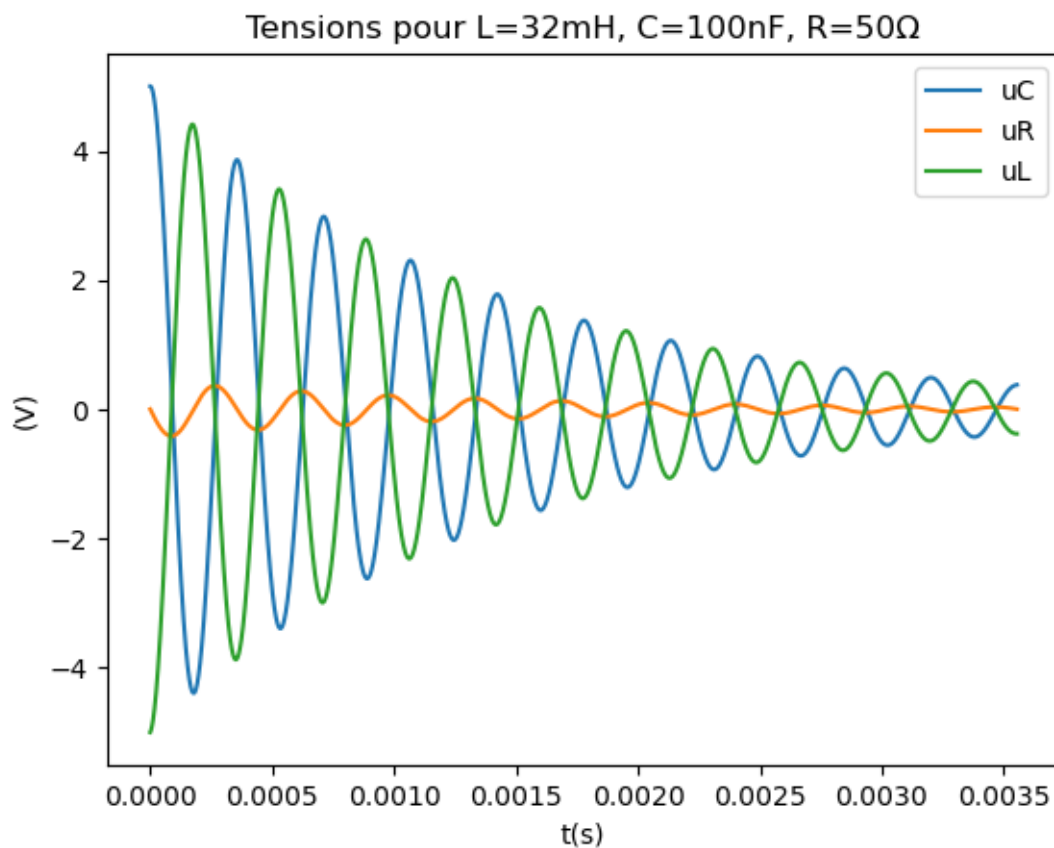

```


[3]: tab_Ec=0.5*C*tab_uc**2
tab_El=0.5*L*tab_i**2
tab_E=tab_Ec+tab_El
plt.figure()
plt.plot(tab_t,tab_Ec,label="Ec")
plt.plot(tab_t,tab_El,label="El")

```

```

plt.plot(tab_t, tab_E, label="E")
plt.legend()
plt.ylabel("(J)")
plt.xlabel("t(s)")
plt.title("Énergies pour L=32mH, C=100nF, R=50Ω")
plt.show()

```

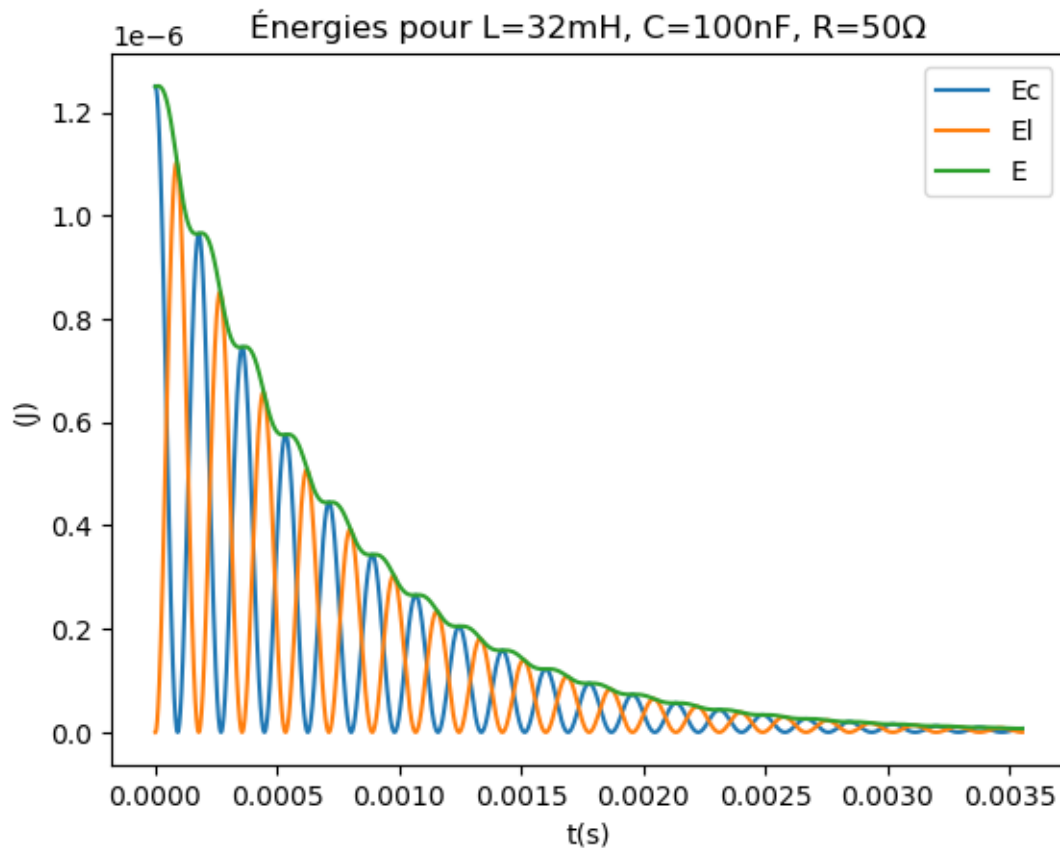

```


[4]: R=0
for i in range(N):
    tab_t[i+1]=tab_t[i]+pas
    tab_uc[i+1]=tab_uc[i]+pas*tab_ducdt[i]
    tab_ducdt[i+1]=tab_ducdt[i]+pas*derivee2(tab_uc[i],tab_ducdt[i],tab_t[i])
tab_i=C*tab_ducdt
tab_ur=R*tab_i
tab_ul=-tab_uc-tab_ur
plt.figure()
plt.plot(tab_t,tab_uc,label="uC(V)")
plt.plot(tab_t,tab_ur,label="uR(V)")
plt.plot(tab_t,tab_ul,label="uL(V)")


```

```

plt.legend()
plt.xlabel("t(s)")
plt.ylabel("(V)")
plt.title("Tensions pour L=32mH, C=100nF, R=0Ω")
tab_Ec=0.5*C*tab_uc**2
tab_El=0.5*L*tab_i**2
tab_E=tab_Ec+tab_El
plt.figure()
plt.plot(tab_t,tab_Ec,label="Ec(J)")
plt.plot(tab_t,tab_El,label="El(J)")
plt.plot(tab_t,tab_E,label="E(J)")
plt.legend()
plt.xlabel("t(s)")
plt.ylabel("(J)")
plt.title("Énergies pour L=32mH, C=100nF, R=0Ω")
plt.show()

```

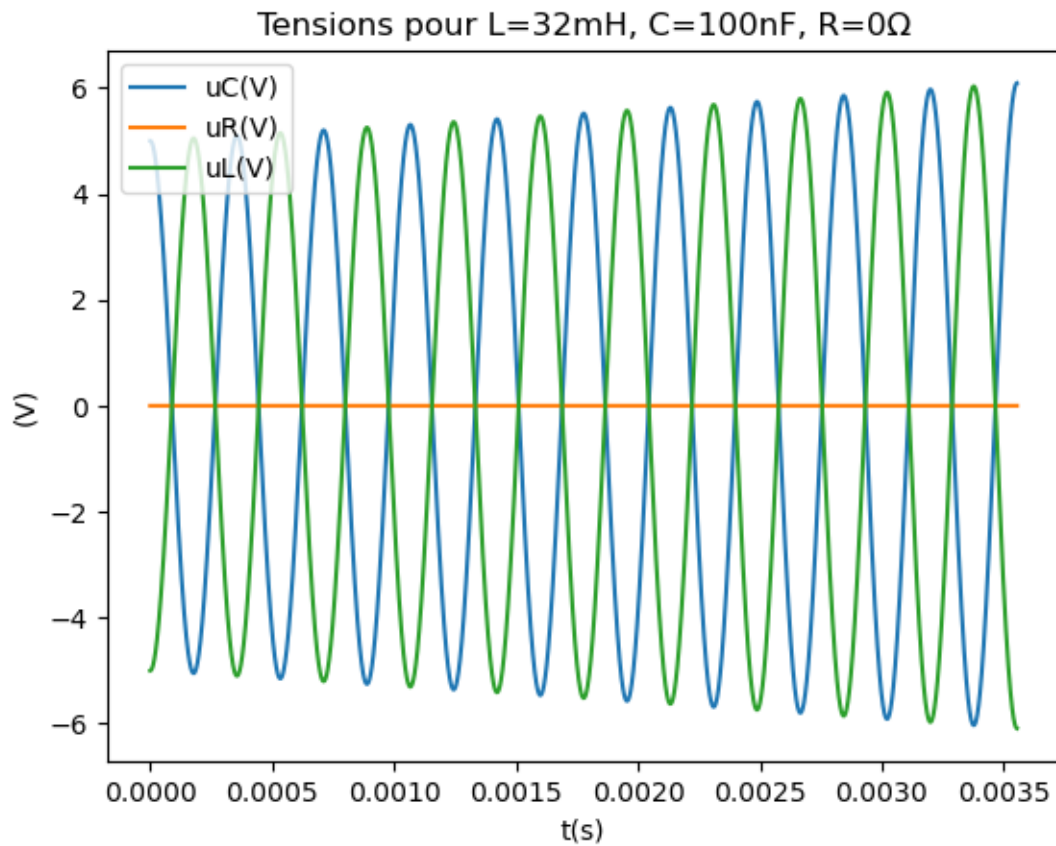

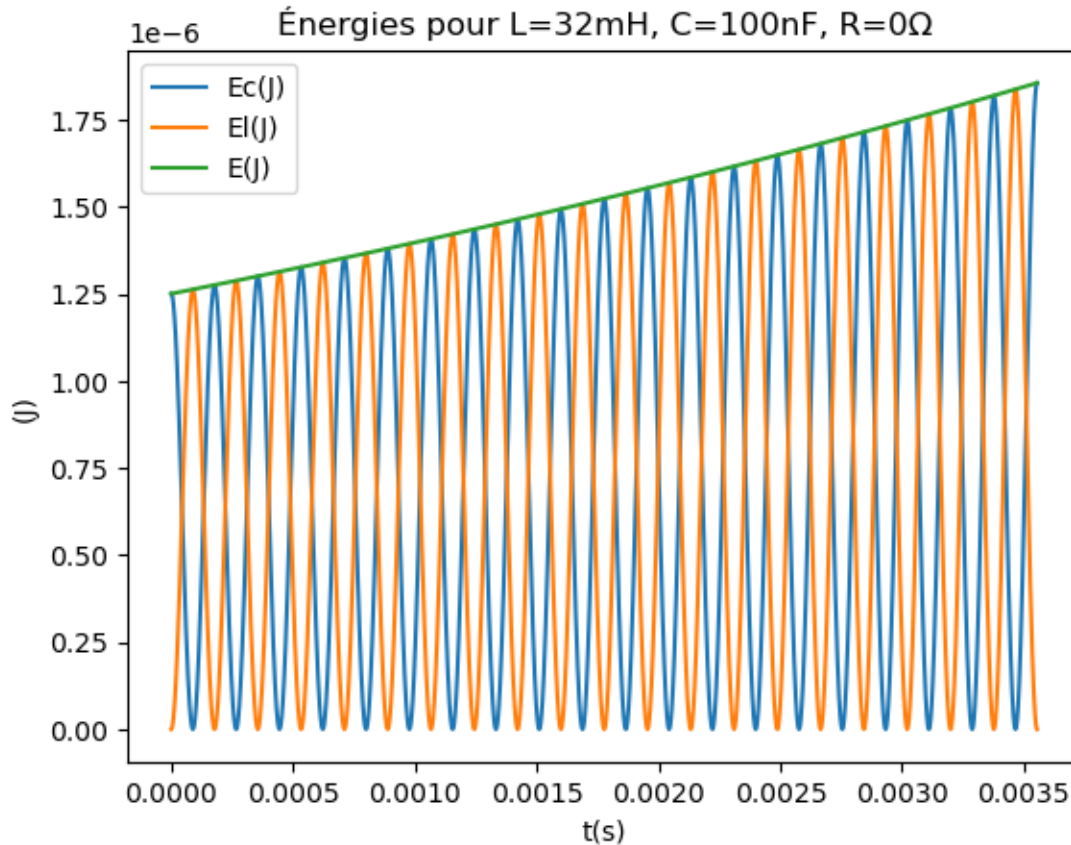

L'énergie augmente! C'est un effet de bord de la méthode d'Euler.


Régime apériodique:


```
[5]: R=1000
for i in range(N):
    tab_t[i+1]=tab_t[i]+pas
    tab_uc[i+1]=tab_uc[i]+pas*tab_ducdt[i]
    tab_ducdt[i+1]=tab_ducdt[i]+pas*derivee2(tab_uc[i],tab_ducdt[i],tab_t[i])
tab_i=C*tab_ducdt
tab_ur=R*tab_i
tab_ul=-tab_uc-tab_ur
plt.figure()
plt.plot(tab_t,tab_uc,label="uC(V)")
plt.plot(tab_t,tab_ur,label="uR(V)")
plt.plot(tab_t,tab_ul,label="uL(V)")
plt.legend()
plt.xlabel("t(s)")
plt.ylabel("(V)")
plt.title("Tensions pour L=32mH, C=100nF, R=1kΩ")
```

```

tab_Ec=0.5*C*tab_uc**2
tab_El=0.5*L*tab_i**2
tab_E=tab_Ec+tab_El
plt.figure()
plt.plot(tab_t,tab_Ec,label="Ec(J)")
plt.plot(tab_t,tab_El,label="El(J)")
plt.plot(tab_t,tab_E,label="E(J)")
plt.legend()
plt.xlabel("t(s)")
plt.ylabel("(J)")
plt.title("Énergies pour L=32mH, C=100nF, R=1kΩ")
plt.show()

```

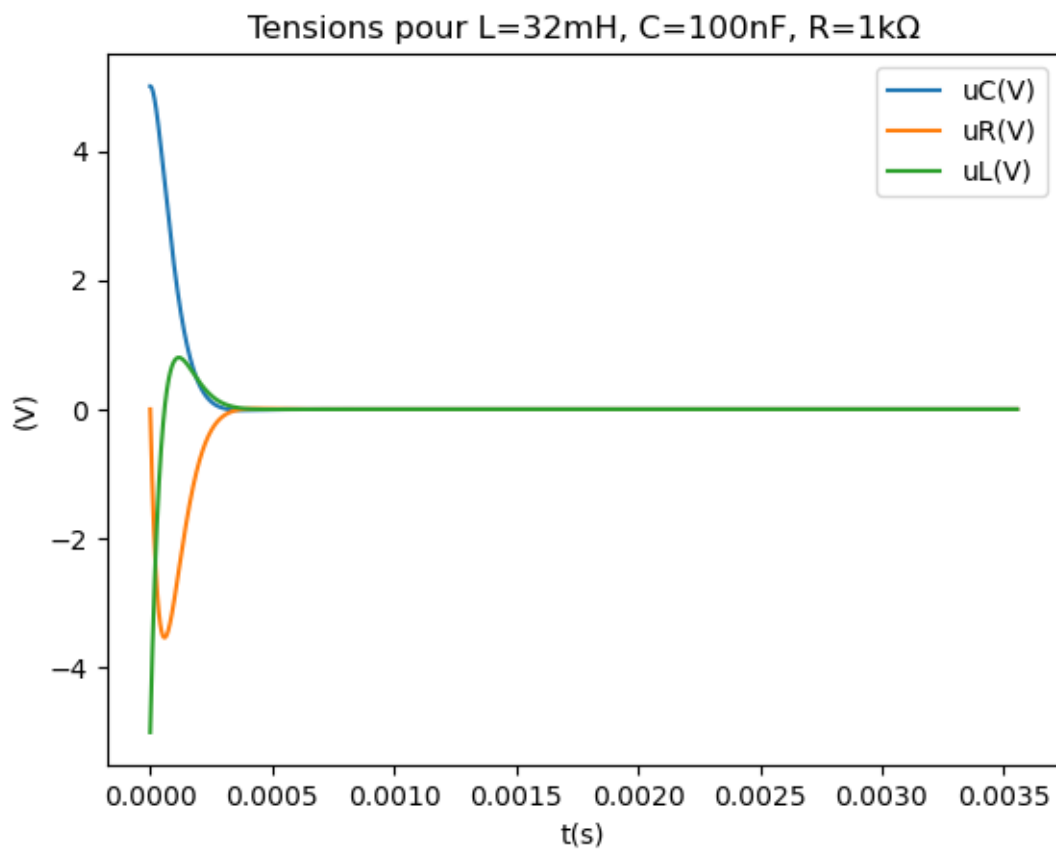

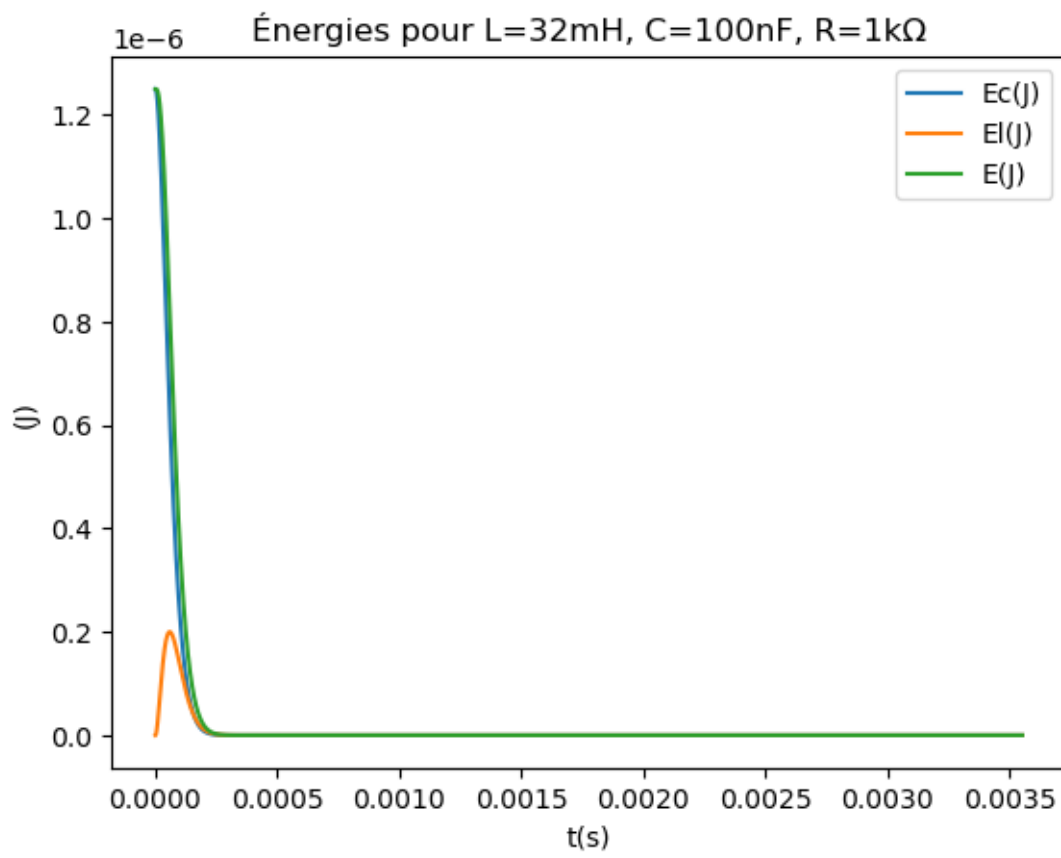

[]:

[]:

[]: