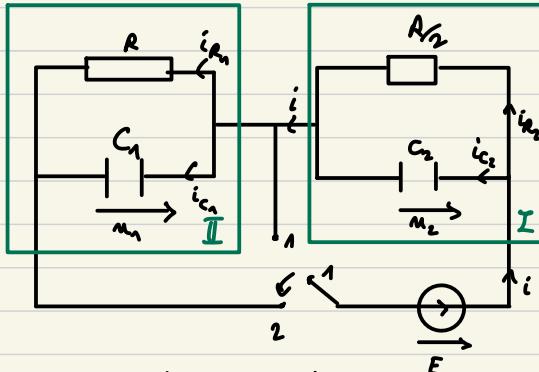


Ex 4:




- $t = 0^-$ :  $C_1$  déchargé (fil)
- $C_2$  chargé (interrupteur ouvert)

Eq° du circuit 1:

$$u_2 = u_R \Rightarrow E = \frac{R}{2} i$$
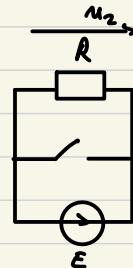
$$\text{à } t = 0^+, \quad u_2 = E, \quad u_R = 0$$



$$E = u_R + u_I$$

Loi des nœuds:

$$\cdot i = i_{C_2} + i_{R_2} = C \frac{du_2}{dt} + \frac{u_2}{R}$$

$$\cdot i = i_{C_1} + i_{R_1} = C \frac{du_1}{dt} + 2 \frac{u_1}{R}$$

$$\Rightarrow \frac{RC}{2} \left[ \frac{du_2}{dt} - \frac{du_1}{dt} \right] + u_2 - \frac{u_1}{2} = 0$$

$$E = u_1 + u_2 \Rightarrow \frac{RC}{2} \left[ \frac{du_2}{dt} - \frac{dE}{dt} + \frac{du_1}{dt} \right] + u_2 - \frac{E}{2} + \frac{u_1}{2} = 0$$

$$\Rightarrow \frac{du_2}{dt} + \boxed{\frac{3}{2RC}} u_2 = \frac{E}{2RC}$$


$$\text{Sol. homogène: } u_{2,H} = A e^{-t/\tau}$$

$$\text{Sol. part.: } u_{2,p} = \frac{E}{3}$$

$$\text{d'où finalement: } u_2 = A e^{-t/\tau} + \frac{E}{3}$$

$$\text{or } u_2(t=0) = E \Rightarrow u_2 = \frac{E}{3}(2e^{-t/\tau} + 1)$$

Ex 2:

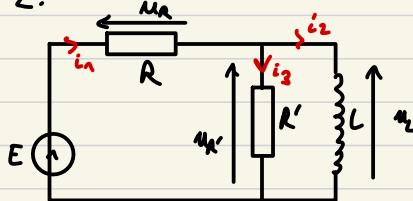

$$1) \text{ Loi des nœuds: } i_1 = i_2 + i_3$$

$$\text{Loi des mailles: } E = u_R + u_L$$

$$u_R = u_L = L \frac{di_2}{dt}$$

$$\begin{aligned} \Rightarrow E &= R i_1 + L \frac{di_2}{dt} \\ &= R i_2 + R i_3 + L \frac{di_2}{dt} \\ &= R i_2 + \underbrace{\frac{R}{R'} R' i_3}_{R+R'} + L \frac{di_2}{dt} \end{aligned}$$

$$\Rightarrow E = R i_2 + \underbrace{\left( \frac{R}{R'} + 1 \right)}_{R+R'} L \frac{di_2}{dt}$$

$\downarrow$

d'où  $\frac{di_2}{dt} + \boxed{\frac{RR'}{(R+R')L} i_2} = \frac{ER'}{(R+R')L}$

$$2) i_2(t) = A e^{-t/\tau} + B \quad \text{Pan corr. du courant}$$

$$i_2(0) = 0 \Rightarrow A + B = 0 \quad \text{d'où } i_2(t) = B(1 - e^{-t/\tau})$$


$$\text{et } \frac{R}{\tau} < \frac{E}{R} \quad \text{d'où } B = \frac{E}{R}$$

$$\text{d'où } i_2(t) = \frac{E}{R}(1 - e^{-t/\tau})$$


$$3) \quad m_{R'} = m_e$$

$$\text{dann} \quad R' i_3(t) = L \frac{di_2}{dt} = \frac{E}{R} e^{-t/\tau}$$

$$\text{dann} \quad i_3(t) = \frac{E}{R+\tau L} e^{-t/\tau}$$

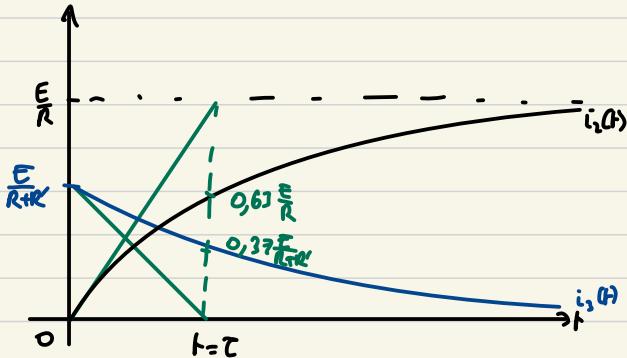

Ex 3:

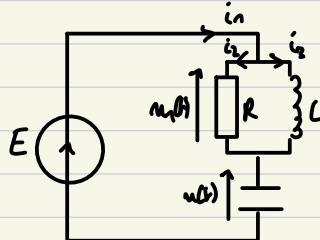

Kirchhoff's laws:

$$E = u_1(t) + u_2(t) \Rightarrow u_1(t) = E - u_2(t)$$

Kirchhoff's laws:

$$i_1 = i_2 + i_3$$

$$\Rightarrow C \frac{du_2(t)}{dt} = \frac{u_1(t)}{R} + i_3$$

$$\Rightarrow C \frac{d^2 u_2(t)}{dt^2} = \frac{1}{R} \frac{du_1(t)}{dt} + \frac{di_3}{dt} / \frac{U_1}{L}$$

$$\Rightarrow C \frac{d^2 u_2(t)}{dt^2} + \frac{1}{LC} u_2(t) + \frac{1}{RC} \frac{du_1(t)}{dt} = \frac{E}{LC}$$

$$\omega_0^2 = \frac{1}{LC} \quad \text{et} \quad \frac{u_1}{\alpha} = \frac{1}{RC}$$

$$\text{i.e.} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad \text{et} \quad \Omega = R \sqrt{\frac{C}{L}}$$

- Sol. part:  $E$
- Sol. générale:  $Q \stackrel{AN}{=} 10 > \frac{1}{2}$ .
- Eq canon:  $x^2 + \frac{\omega_0^2}{\alpha} x + \omega_0^2 = 0$

de divise:

$$\begin{aligned}\Delta &= \frac{\omega_0^2}{\alpha^2} - 4\omega_0^2 < 0 \\ &= -4\omega_0^2 \left(1 - \frac{1}{4Q^2}\right) \\ &= (i2\omega_0\sqrt{1-\frac{1}{4Q^2}})^2\end{aligned}$$

et:  $x_{1,2} = -\frac{\omega_0}{2\alpha} \pm i\omega_0\sqrt{1-\frac{1}{4Q^2}}$

on pose ici:  $\cdot \vartheta = \omega_0\sqrt{1-\frac{1}{4Q^2}}$   
 $\cdot \tau = \frac{2\alpha}{\omega_0}$

on a:  $x_{1,2} = -\frac{1}{\tau} \pm i\vartheta$ .

et:

$$u(t) = e^{-\frac{t}{\tau}} U_0 \cos(\vartheta t + \varphi) \quad \vartheta \in \mathbb{R}.$$

donc  $\underline{u_{gen}(t) = U_0 e^{-\frac{t}{\tau}} \cos(\vartheta t + \varphi) + E_0}$ .

Réponse filtre d'ordre 2:

pour  $H = \frac{1}{1 - \frac{\omega^2}{\omega_0^2} + j\frac{\omega}{\alpha\omega_0}}$


$$\omega = \frac{\omega}{\omega_0}, \quad H = \frac{1}{1 - \omega^2 + j\frac{\omega}{\alpha}}$$

$$H(z) \underset{z \rightarrow 0}{\sim} 1, \quad H(z) \underset{z \rightarrow \infty}{\sim} -\frac{1}{z^2}$$

→ passe bas.

$$G_{dB} = 20 \log(|H|),$$
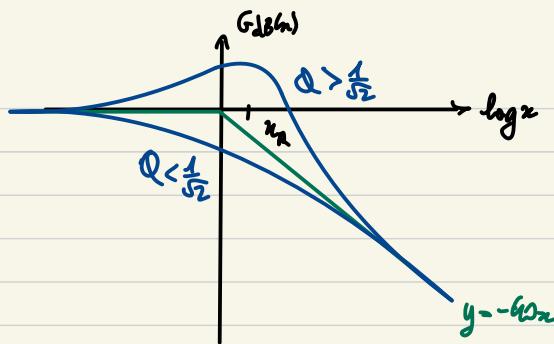
$$G_{dB}(z \rightarrow 0) = 0, \quad G_{dB}(z \rightarrow \infty) = -6 \log(\alpha).$$



$$\omega_L = \omega_0 \sqrt{1 - \frac{1}{2Q^2}}$$