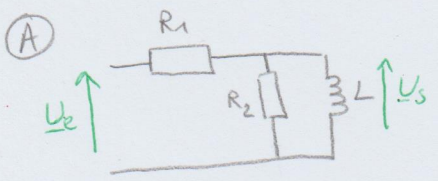



Exercise 4



Q1: BF: HF:
 $\frac{U_3}{U_e} = 0$ $\frac{U_3}{U_e} = \frac{R_2}{R_1 + R_2}$
 → **filtre passe haut**

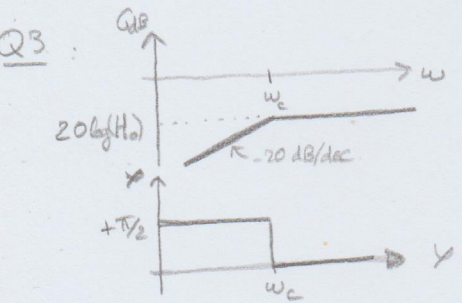Q2:
$$\underline{H}(j\omega) = \frac{U_3}{U_e} = \frac{j\omega L \cdot R_2}{R_1 + j\omega L \cdot R_2} = \frac{R_2}{R_1 + R_2} \times \frac{j\omega L \cdot \frac{R_1 R_2}{R_1 + R_2}}{1 + j\omega L \cdot \frac{R_1 R_2}{R_1 + R_2}}$$


$$\underline{H}(j\omega) = H_0 \times \frac{j\frac{\omega}{\omega_c}}{1 + j\frac{\omega}{\omega_c}} \quad \text{avec} \quad \begin{cases} H_0 = \frac{R_2}{R_1 + R_2} \\ \omega_c = \frac{R_1 R_2}{R_1 + R_2} \cdot \frac{1}{L} \end{cases}$$



Q4: on cherche $Q(\omega) = \frac{G_{max}}{\sqrt{2}}$ ou $G_{dB} = G_{dB_{max}} - 3dB$
 $G = H_0 \cdot \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + (\frac{\omega}{\omega_c})^2}} \rightarrow G_c = \frac{H_0}{\sqrt{2}} \rightarrow \omega = \omega_c$
 AN: $\omega_c = 13,1 \text{ krad.s}^{-1}$
 $f_c = 209 \text{ kHz}$
 BP = $[\omega_c, +\infty[$

Q5: $U_e(t) = \text{cte} \Rightarrow \omega \rightarrow 0 \Rightarrow U_s(t) = 0$
Q6: $U_e(t) = U_0 \cdot (1 + \cos(2\pi f_1 \cdot t))$
 on traite chaque composante indépendamment
 $U_s(t) = 0 + U_0 \cdot G(f_1) \cdot \cos(2\pi f_1 \cdot t + \varphi(f_1))$
 $\rightarrow U_s(t) = U_0 \times 37,5 \times 10^{-3} \cdot \cos(2\pi f_1 \cdot t + 1,47)$

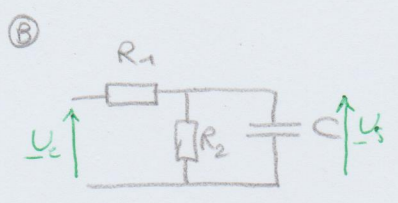
Q7: $U_e(t) = U_0 + U_0 \cdot \cos(2\pi f_1 \cdot t) + U_0 \cdot \cos(2\pi f_2 \cdot t + \frac{\pi}{4}) + U_0 \cdot \cos(2\pi f_3 \cdot t + \frac{\pi}{3})$
 $\rightarrow U_s(t) = 0 + 0 + U_0 \cdot 0,97 \cdot \cos(2\pi f_1 \cdot t + 1,3) + U_0 \cdot 0,33 \cdot \cos(2\pi f_2 \cdot t + 0,99)$
 (Note: terms are negligible)



Q1: BF: HF:
 $\frac{U_3}{U_e} = \frac{R_2}{R_1 + R_2}$ $\frac{U_3}{U_e} = 0$
 → **filtre passe bas**

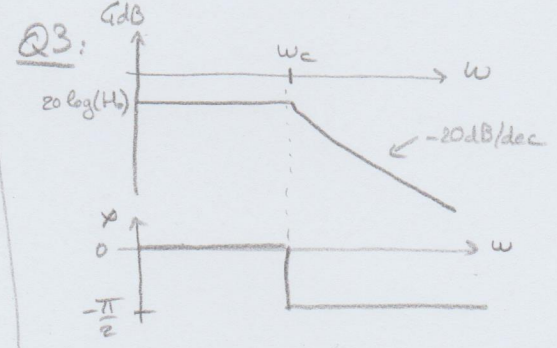Q2:
$$\underline{H}(j\omega) = \frac{R_2}{R_1 + R_2} \times \frac{1}{1 + j\omega C \cdot \frac{R_1 R_2}{R_1 + R_2}}$$

$$= H_0 \times \frac{1}{1 + j\frac{\omega}{\omega_c}} \quad \text{avec} \quad \begin{cases} H_0 = \frac{R_2}{R_1 + R_2} \\ \omega_c = \frac{R_1 R_2}{R_1 + R_2} \cdot C \end{cases}$$



Q4: $G_c = \frac{H_0}{\sqrt{2}} \rightarrow \omega = \omega_c$
 BP = $[0, \omega_c]$
 AN: $\omega_c = 4,7 \text{ rad.s}^{-1}$
 $f_c = 2 \text{ Hz}$

Q5: $U_e(t) = \text{cte} \Rightarrow \omega \rightarrow 0 \Rightarrow U_s(t) = H_0 \cdot U_e(t) = 0,33 \times U_e(t)$

Q6: $U_e(t) = U_0(1 + \cos(2\pi f_1 \cdot t))$
 $U_s(t) = U_0 + 4 \times 10^{-3} \cdot U_0 \cdot \cos(2\pi f_1 \cdot t + \frac{\pi}{2})$
 $U_s(t) \approx U_0$ (negligible)
 → **filtre moyennneur**

Q7: pour la même raison
 $U_s(t) \approx U_0$