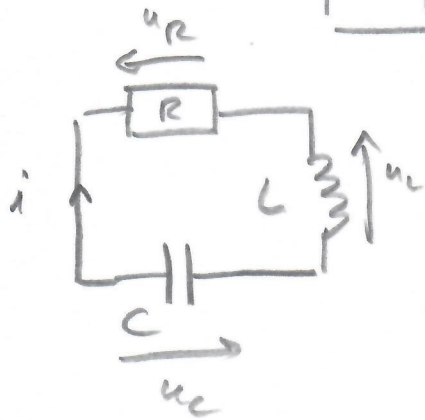




loi des mailles: $u_R + u_L + u_C = 0$

$$Ri + L \frac{di}{dt} + u_C = 0$$

On a: $i = C \frac{du_C}{dt}$

$$LC \frac{d^2 u_C}{dt^2} + RC \frac{du_C}{dt} + u_C = 0$$

On a encore

$$\ddot{u}_C + \frac{R}{L} \dot{u}_C + \frac{1}{LC} u_C = 0 \quad (*)$$

$$\frac{\omega_0}{\alpha} = \frac{R}{L}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$Q = \frac{L}{\sqrt{LC}} \frac{1}{R}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

AN: $\omega_0 = \frac{1}{\sqrt{4 \cdot 10^{-6} \cdot 10^{-2}}} = \frac{1}{2 \cdot 10^{-4}} = 5 \cdot 10^3 \text{ rad.s}^{-1}$

$$Q = \frac{1}{100} \sqrt{\frac{10^{-2}}{4 \cdot 10^{-6}}} = \frac{1}{100} \frac{\sqrt{10^4}}{\sqrt{C}} = \frac{1}{2}$$

Résolution(*):

$$r^2 + \frac{\omega_0}{\alpha} r + \omega_0^2 = 0$$

$$\Delta = \left(\frac{\omega_0}{\alpha}\right)^2 - 4\omega_0^2 = \omega_0^2 \left(\frac{1}{Q^2} - 4\right) = 0$$

$\Delta = 0 \rightarrow$ régime critique

$$r_0 = -\frac{\omega_0}{2Q} = -\omega_0 = -\frac{1}{\tau} \quad (2Q=1)$$

C Vac III - 1

$$dr \quad | u_c(t) = (At + B) e^{-\omega_0 t}$$

$$\underline{\text{À } t=0,} \quad u_c(t=0^+) = u_c(t=0^-) = E$$

$$u_c(0) = B = E$$

$$\text{Donc } u_c(t) = (At + B) e^{-\omega_0 t}$$

$$i = C \frac{du_c}{dt} = C [A - \omega_0 (At + B)] e^{-\omega_0 t}$$

$$i(0) = 0 \quad \text{pas continuité du courant dans la bobine}$$

$$i(0) = C [A - \omega_0 B] = 0$$

$$| A = \omega_0 B = \omega_0 E |$$

Donc au final:

$$| u_c(t) = E(1 + \omega_0 t) e^{-\omega_0 t} |$$