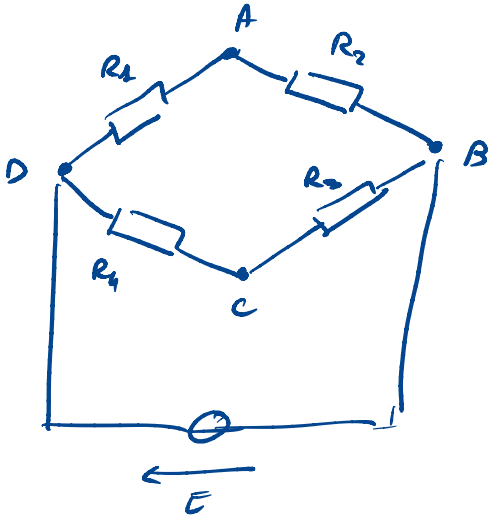


Exercice 5 Wheatstone.

1)



$$U_{AB} = \frac{R_2}{R_1 + R_2} E \quad (\text{Pdt})$$

$$U_{CB} = \frac{R_4}{R_1 + R_3} E$$

$$U_{AC} = V_A - V_C = V_A - V_B + V_B - V_C$$

$$U_{AC} = U_{AB} - U_{BC}$$

$$U_{AC} = \left(\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_1 + R_3} \right) E$$

or $U_{AC} = 0$ car le pont est équilibré

$$\text{donc } \frac{R_2}{R_1 + R_2} = \frac{R_4}{R_1 + R_3}$$

$$\cancel{R_2 R_1} + R_2 R_3 = R_1 R_4 + \cancel{R_2 R_1}$$

$$\boxed{R_2 R_3 = R_1 R_4}$$

2) $R_4 = \frac{R_2 R_3}{R_1}$

A.W. $R_4 = \frac{150 \times 200}{100} = 300 \Omega$

[3] cf Q1
$$U_{AC} = \left(\frac{R_2}{R_1 + R_2} - \frac{R_1}{R_3 + R_4} \right) E$$